

Final Project Report

SOC Design 系統晶片設計


Group 7

112061603 李柏叡

112061620 郭邑哲


112061621 貢暉家

一、Block diagram :

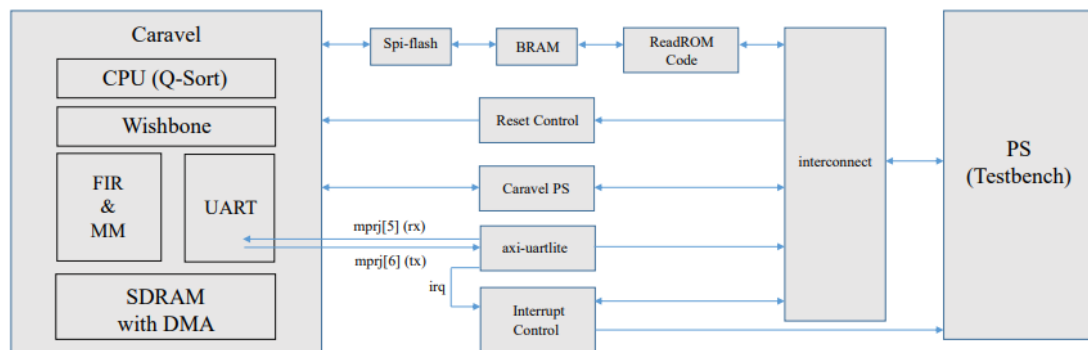

二、DMA&Arbiter :


- DMA&Arbiter diagram:

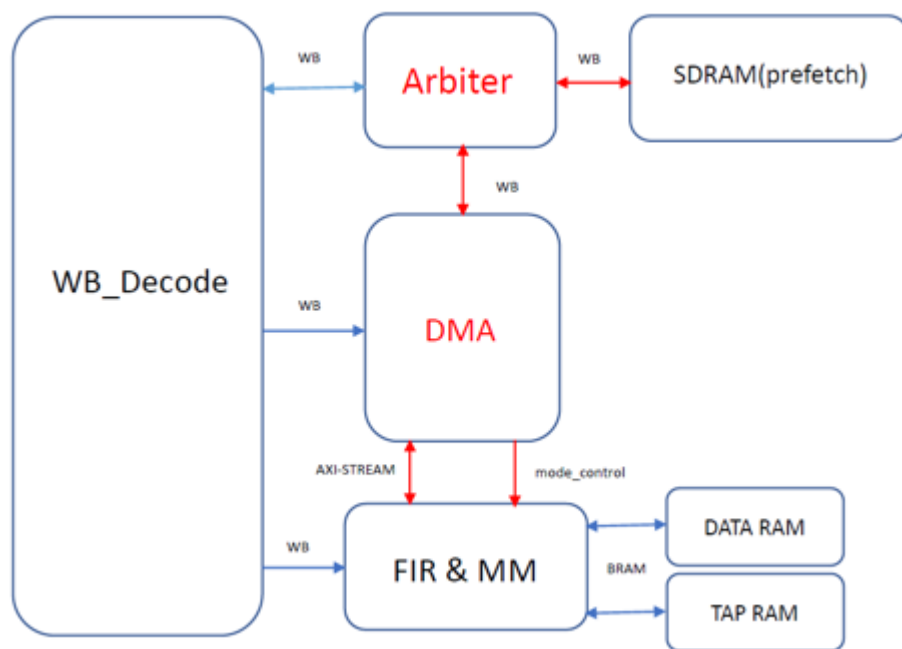

- 1 input buffer and 1 output buffer:


Input buffer:

 S_0 : Idle
 S_1 : wait Fir_MM read ($ss_tdata = Inputbuffer$)
 S_2 : pull read request to SDRAM ($Inputbuffer = SDRAM_data_0$)



Output buffer:

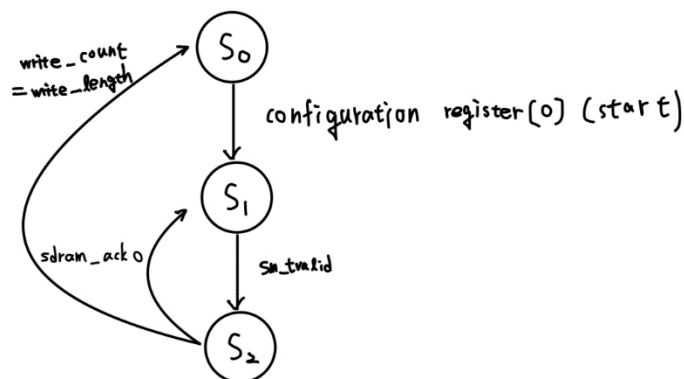S_0 : Idle
 S_1 : wait Fir_MM write ($Outputbuffer = sm_tdata$)
 S_2 : pull write request to SDRAM ($SDRAM_data_i = Outputbuffer$)



- DMA Configuration register map:


When the fir_mm hardware requires data, it does not rely on the CPU for data read or write operations. Instead, it can directly access memory through DMA, thereby accelerating computation speed and enhancing memory access efficiency.

| address | bit | |
|------------|--------|------------------------|
| 0X380002AC | [0] | Start |
| | [1] | Idle |
| 0X380002B0 | [31:0] | Read starting address |
| 0X380002B4 | [31:0] | Read length |
| 0X380002B8 | [31:0] | Write starting address |
| 0X380002BC | [31:0] | Write length |


- **Arbiter:**

The main function of the arbiter is to determine whether DMA or the CPU should access memory at a given moment, enabling concurrent execution of both.

 When DMA and CPU both have requests to memory at the same time, arbiter prioritized handling requests from DMA.




State diagram:

 

三、SDRAM with Pre-fetch :

| User Project SDRAM address map | |
|--------------------------------|-------------------|
| Bank0 | Qsort instruction |
| Bank1 | Fir & MM data |
| Bank2 | Fir & MM data |
| Bank3 | Qsort data |


- SDRAM with Pre-fetch diagram:

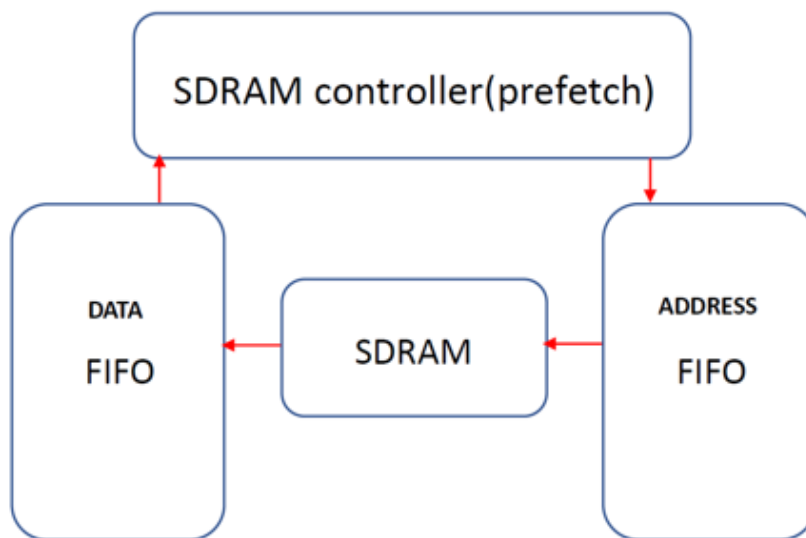


- Waveform view:

In order to implement the prefetch functionality, three prefetch buffers have been introduced. These prefetch buffers are designed to anticipate the next instruction, utilizing the three WAIT states following the READ state. If the prediction is successful, the instruction can be read out after only two clock cycles. However, in case of prediction failure, it still requires 8 cycles, and the system proceeds to the next prefetch.

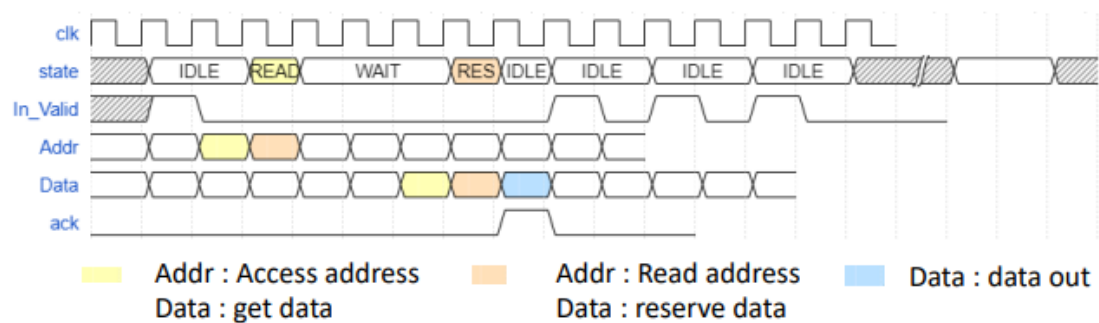
Without Pre-fetch : 32 clocks are required to execute 4 instructions



32cycle

 

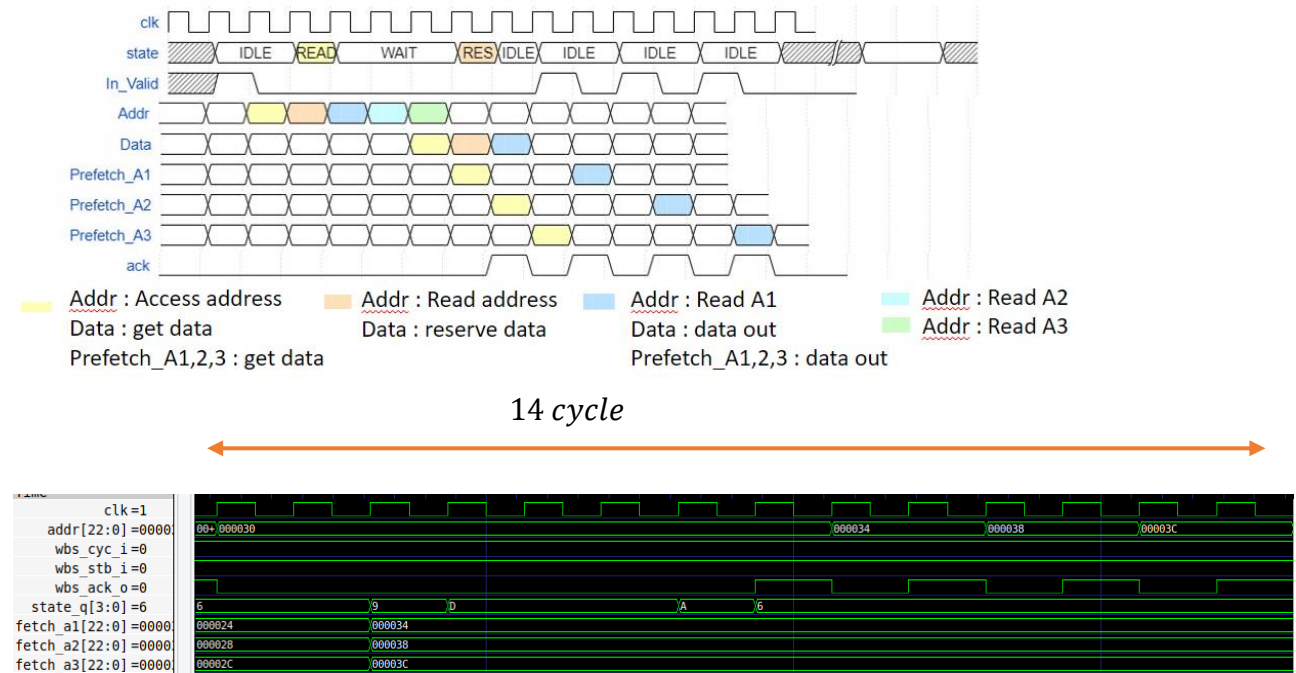With Pre-fetch : 14 clocks are required to execute 4 instructions




四、Fir & Matrix multiplication

Both Fir and Matrix multiplication need multiply-add operation. So, we decided to make an accelerator to do fir and matrix multiplication.


Since we want to store matrix A and matrix B in tap ram and data ram, we set the size of these two RAMs to 16 DW.

- Fir & Matrix multiplication diagram:

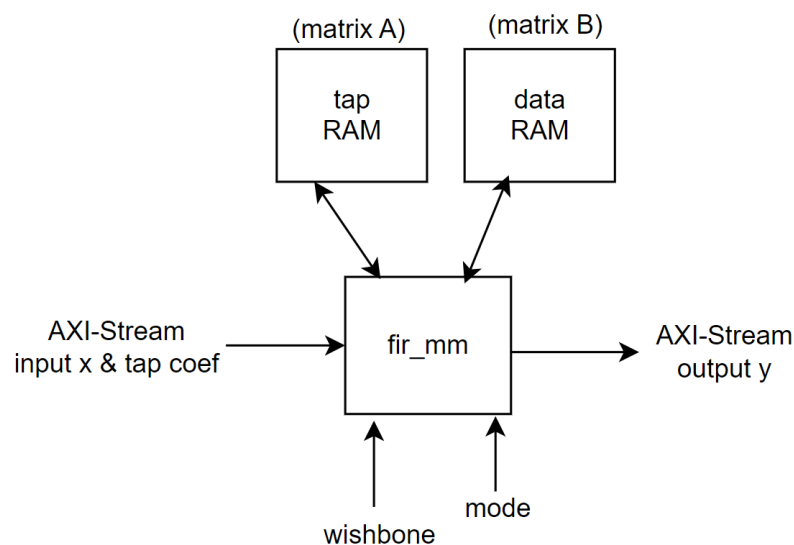

- Fir & Matrix multiplication architecture:

Using 1 multiplier and 1 adder

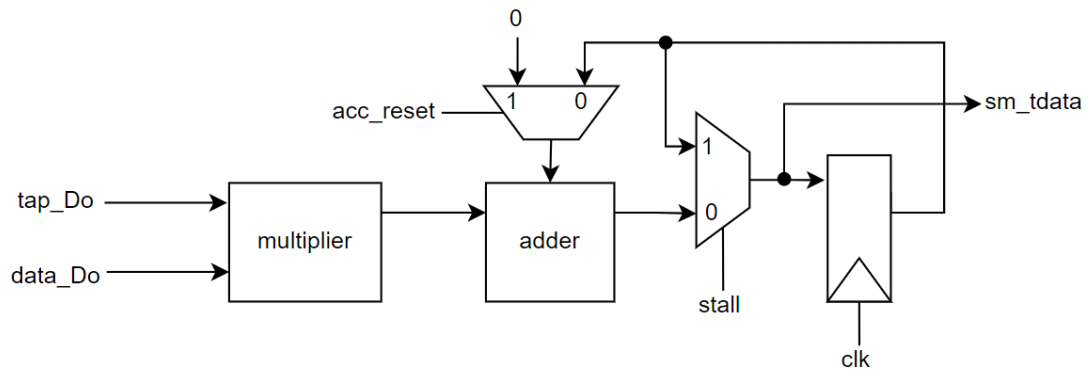


- Fir & Matrix multiplication mode:

- Set tap mode:

Input tap coefficient by using AXI-Stream and store the coefficient in tap RAM .

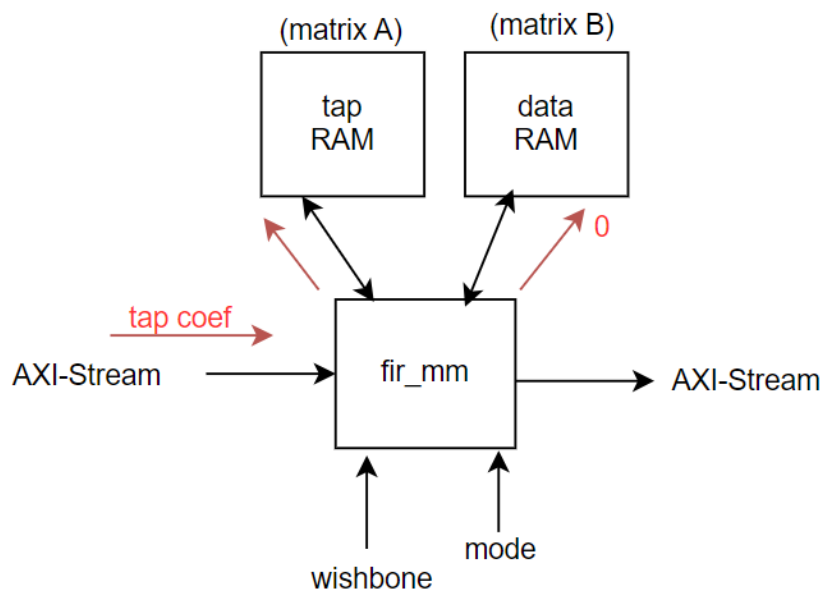Use a counter to count from 0 to 10 (the counter increases when Fir_mm receives 1 coefficient), then Fir_mm returns to IDLE state.



- FIR mode:

--Do Fir (output a data needs 11 cycles)

-- Use three counters:

- Tap_idx: counting the 11 cycles needed to produce 1 output
- Data_idx: count how many input x received, when it reaches data_length, fir_mm return to idle state
- Data_A_shift: used to calculate data_RADDR

III. Matrix multiplication mode:

- Input matrix A and matrix B using AXI-Stream. (max speed: 32 cycles)
- Store matrix A in tap RAM and store matrix B in data RAM.
- After both matrixes are stored in RAM, start the computation.(max speed: 64 cycles)
- Use two counters to determine read address:
Tap_idx : count from 0 to 15, then goes back to 0
Data_idx : starts from 0x010, increase 1 every time tap_idx return to 0

| | | | | | | | |
|-----------------------|------|------|------|------------------------|------|------|------|
| 0000 | 0001 | 0010 | 0011 | 0000 | 0001 | 0010 | 0011 |
| 0100 | 0101 | 0110 | 0111 | 0100 | 0101 | 0110 | 0111 |
| 1000 | 1001 | 1010 | 1011 | 1000 | 1001 | 1010 | 1011 |
| 1100 | 1101 | 1110 | 1111 | 1100 | 1101 | 1110 | 1111 |
| MATRIX_A (tap RAM) | | | | MATRIX_B (data_RAM) | | | |

```
tap_RADDR = {data_idx[2],data_idx[0],tap_idx[1:0]};  
data_RADDR = {tap_idx[1:0],tap_idx[3:2]};
```

IV. Simulation State cycles:

With qsort concurrently executing:

State 1(SET TAP Mode):

92 cycle

State 2(FIR Mode):

916 cycle

State 3(MM Mode):

335 cycle

Total (FIR & MM) finish:

1343 cycle

● Fir & Matrix multiplication synthesis result:

No extra register is needed for the original Fir to support Matrix-multiplication.

| Site Type | Used | Fixed | Prohibited | Available | Util% |
|-----------------------|------|-------|------------|-----------|-------|
| CLB LUTs* | 171 | 0 | 0 | 117120 | 0.15 |
| LUT as Logic | 171 | 0 | 0 | 117120 | 0.15 |
| LUT as Memory | 0 | 0 | 0 | 57600 | 0.00 |
| CLB Registers | 75 | 0 | 0 | 234240 | 0.03 |
| Register as Flip Flop | 75 | 0 | 0 | 234240 | 0.03 |
| Register as Latch | 0 | 0 | 0 | 234240 | 0.00 |
| CARRY8 | 8 | 0 | 0 | 14640 | 0.05 |
| F7 Muxes | 0 | 0 | 0 | 58560 | 0.00 |
| F8 Muxes | 0 | 0 | 0 | 29280 | 0.00 |
| F9 Muxes | 0 | 0 | 0 | 14640 | 0.00 |

● Observation

Adding prefetch buffers to each individual bank enables successful memory access prefetching even when branching across different banks (Due to parallel execution of software and hardware, there is a probability of continuously switching bank address)

Ex: time 0 (qsort) → time 1 (FIR and MM) → time 2 (FIR and MM) → time 3 (qsort)

38000300 → 38000100 → 38000104 → 38000304

single bank prefetch buffer:

| | buffer 0 | buffer 1 | buffer 2 | buffer 3 | |
|--------------|----------|---|----------|----------|---------|
| time 0 : | 38000300 | 38000304 | 38000308 | 3800030C | 8 cycle |
| miss ↓ flush | | | | | |
| time 1 : | 38000100 | 38000104 | 38000108 | 3800010C | 8 cycle |
| hit ↓ | | | | | |
| time 2 : | 38000100 | 38000104 hit | 38000108 | 3800010C | 2 cycle |
| miss ↓ flush | | | | | |
| time 3 : | 38000304 | 38000308 | 3800030C | 38000310 | 8 cycle |

four individual bank prefetch buffer:

| | bank3 - buffer 0 | bank3 - buffer 1 | bank3 - buffer 2 | bank3 - buffer 3 | |
|----------|------------------|---|------------------|------------------|---------|
| time 0 : | 38000300 | 38000304 | 38000308 | 3800030C | 8 cycle |
| ↓ | | | | | |
| time 1 : | bank1 - buffer 0 | bank1 - buffer 1 | bank1 - buffer 2 | bank1 - buffer 3 | 8 cycle |
| hit ↓ | | | | | |
| time 2 : | 38000100 | 38000104 hit | 38000108 | 3800010C | 2 cycle |
| hit ↓ | | | | | |
| time 3 : | bank3 - buffer 0 | bank3 - buffer 1 | bank3 - buffer 2 | bank3 - buffer 3 | 2 cycle |
| | 38000300 | 38000304 hit | 38000308 | 3800030C | |

Number of cycles required to finish FIR MM QSORT:

Single bank prefetch buffer : 6652 cycle

Four individual bank prefetch buffer : 5773 cycle

- FPGA result

[illegible]

- Github link

<https://github.com/ruei7916/SOC-final-project>